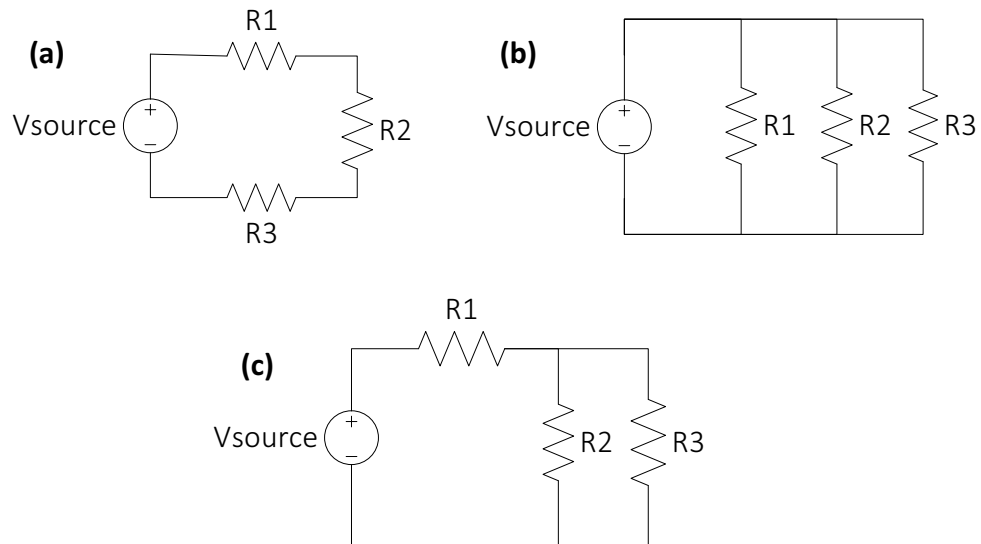


# EECE.2160: ECE Application Programming

## Programming Assignment #2: Basic I/O and Operations

### Figures



**Figure 1:** Basic three-resistor circuits, showing **(a)** all three resistors in series, **(b)** all three resistors in parallel, and **(c)** two of the resistors in parallel, with a third in series with each.

## Circuit Analysis Supplement


The basic equations needed for this program are shown below in Figure 2. For more details on the analysis of series/parallel circuits, contact your instructor directly.

In all cases, given  $x = 1, 2$ , or  $3$ :

$V_x$  = voltage drop across resistor  $R_x$   
(for example,  $V_1$  = voltage across  $R_1$ )


$I_x$  = current through resistor  $R_x$   
(for example,  $I_3$  = current through  $R_3$ )

### SERIES CIRCUIT

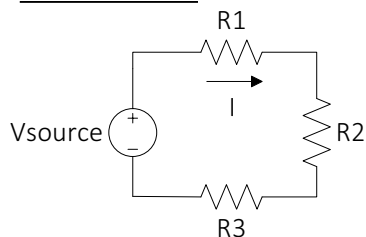

$$\begin{aligned} R_{\text{total}} &= R_1 + R_2 + R_3 \\ I &= V_{\text{source}} / R_{\text{total}} \\ &= I_1 = I_2 = I_3 \text{ (all currents equal)} \\ V_x &= I * R_x \end{aligned}$$


### PARALLEL CIRCUIT

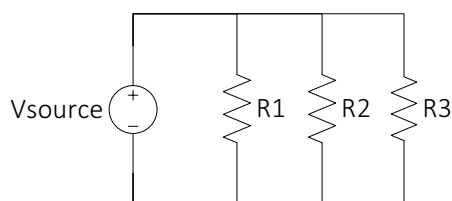

$$\begin{aligned} V_{\text{source}} &= V_1 = V_2 = V_3 \text{ (voltage across all resistors equal)} \\ I_x &= V_{\text{source}} / R_x \end{aligned}$$
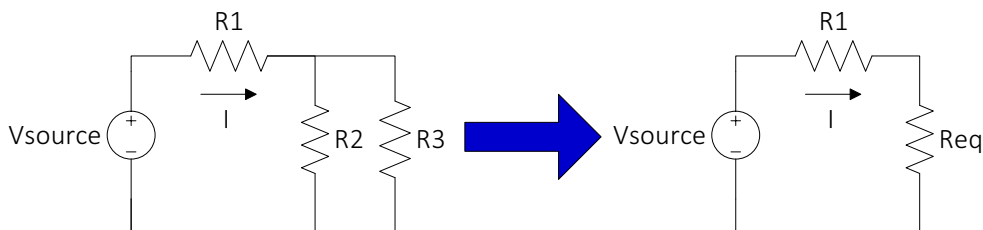
### SERIES/PARALLEL COMBINATION

To solve for all voltages/currents, convert the original circuit to the equivalent circuit on the right



$$\begin{aligned} R_{\text{eq}} &= \text{single resistance equivalent to parallel combination of } R_2, R_3 \\ &= (R_2 * R_3) / (R_2 + R_3) \\ I &= V_{\text{source}} / (R_1 + R_{\text{eq}}) \\ V_{\text{eff}} &= I * R_{\text{eq}} \\ V_1 &= I * R_1 \\ V_2 = V_3 &= V_{\text{eff}} \text{ (voltage across parallel resistors is the same)} \\ I_1 &= I \\ I_2 &= V_{\text{eff}} / R_2 \\ I_3 &= V_{\text{eff}} / R_3 \end{aligned}$$

**Figure 2:** Circuit diagrams with equations for analyzing each circuit